

# AVO CT 160 Modifications

Karsten Simon 07/2012

The modifications described here were made on a CT160 with serial number ACW330LB. I had purchased this unit about a year ago from a gentleman in Eindhoven/Netherlands. Except for the original power cord socket which had been replaced by a standard IEC type and a poorly repainted case the cosmetic appearance looked acceptable. Back at home a closer inspection revealed:

- Partially burnt Grid voltage potentiometer RV2. The pot still worked but the coil body was deformed by the heat and did not look very trustworthy.
- Worn out Anode current backing off potentiometer RV4. Even after disassembling, cleaning and lubricating all the wipers and contact areas with contact grease contacting remained unreliable.
- RL1 winding on protective relay and light bulb LP2 open.

I decided to repair these defects, to replace the EB91 with silicon diodes and to partially rework the original circuit.

## Basic Circuit and Modifications

I relied much on the circuit diagram drawn by Martin Forsberg, his elaborate explanations in the forum (<http://www.vintage-radio.net/forum/showthread.php?t=58088>) and other private information from him.

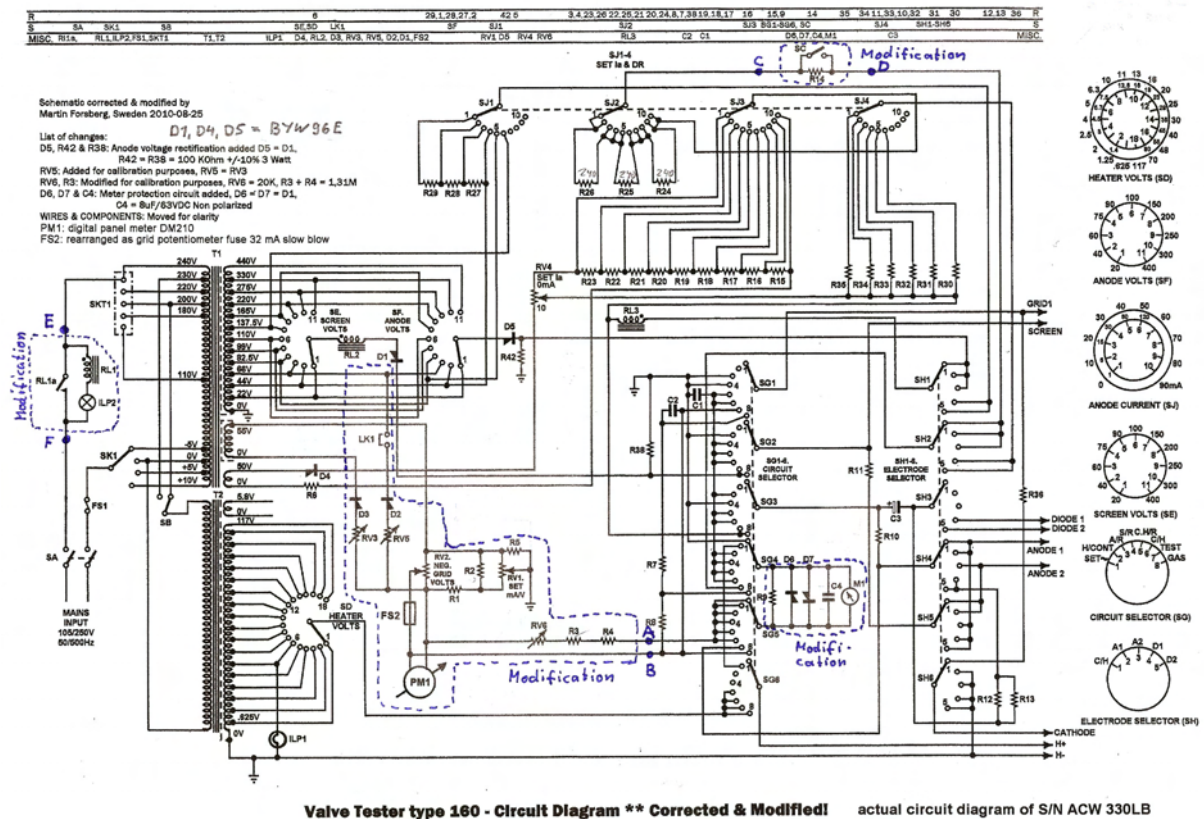


Fig. 1 – Diagram of original circuit with indicated areas of modification



The analogue meter reads full scale at  $97.5 \text{ mV} = 100 \text{ scale divisions}$  on the  $\mu\text{A Ig}$  scale. For easy comparison the DVM should also display "100.0" at analogue meter full scale deflection. Rather than employing a disproportionately elaborate op amp circuit this small difference of  $2.5 \text{ mV}$  is made up for by a single  $60 \text{ Ohm}$  resistor in series with the  $10 \text{ KOhm}$  shunt resistor R9. Without the resistor large values show a discernible difference between analogue and digital readings and will tempt you to fiddle with the mechanical zero screw.

The error caused by this small series resistor can be eliminated by proper alignment on all measuring functions except Anode current backing off. Here the reading error for the  $1 \text{ mA/V}$  mark caused by the additional series resistor is  $+1.75\%$ . However, the internal resistance of the 9 position bridge ladder R15 ... R23 is compensated by only three grouped resistors R24 ... R26 which already causes an inherent error of  $\pm 2.4\%$  for the  $1 \text{ mA/V}$  reading. AVO states the overall accuracy of the tester as  $\pm 5\%$ . So the additional  $+1.75\%$  will shift the overall error to  $\pm 5\% + 1.75\% = -3.25\% \dots +6.75\%$  which is negligible in practical work.

### **Analogue Meter Protection**

The meter is protected by a damping capacitor and four clamping diodes as described in the forum thread <http://www.vintage-radio.net/forum/showthread.php?t=55782&page=3> .

### **Calibration Voltage**

The half wave rectified negative calibration voltage is taken from the  $99 \text{ V}$  and  $137.5 \text{ V}$  taps of T1 via a  $10 \text{ KOhm}$  trimpot. The circuit is similar to the one in the CT160A. At nominal mains voltage (use a variac) the trimpot is adjusted to the SET  $\sim$  mark ( $= 90\% \text{ f.s.}$ ) on the analogue meter = "90.0" on the digital panel meter.

### **Replacement of Backing Off Potentiometer**

The worn out wire wound  $90 \text{ Ohm}$  potentiometer was replaced by a conductive plastic type with  $100 \text{ Ohm}$  nominal resistance. It actually measured  $95 \text{ Ohm}$ . Excel Linear Regression yielded a  $730 \text{ Ohm}$  parallel resistor as optimum to bring its setting into accurate alignment with the etched markings on the panel.

In practical use the conductive plastic potentiometer has turned out to be superior to the original wire wound type in terms of sensitivity and setting precision, probably because of its inherently infinite resolution.

### **Direct Measurement of Anode Current**

Resistor R14 was replaced by a  $5 \text{ KOhm}$  and a  $500 \text{ KOhm}$  trimpot in series. The  $500 \text{ KOhm}$  trimpot can be switched out by a normally open pushbutton contact on the front panel. With the  $\text{mA/V}$  dial parked and the anode current backing off controls at zero the trimpots are adjusted to  $10 \text{ mA f.s.}$  with pushbutton depressed ( $100 \text{ mA f.s.}$  with button released). This modification greatly assists in backing off an unknown anode current and avoids the need for an external meter in most cases.

A similar modification has been described in the forum by Craig Sawyers:

<http://www.vintage-radio.net/forum/showthread.php?t=78402&highlight=ct160> .

### **Overload Relay and Red Lamp LP2**

The open relay coil RL1 was rewound by a professional electric motor repair shop. The lamp was replaced by a Paulmann type 800.11.

A W08M bridge rectifier was inserted between the relay contact and the RL1 – LP2 series circuit. This greatly reduces contact arcing but also makes relay action rather quiet. However, whenever the relay contact moves the digital display begins to flicker and show irregular values. This catches immediate attention and is a good alternative to the former loud relay chatter.

The relay spring carries the full lamp current when the contact opens. This can cause the spring wire to heat up and completely loose its elasticity rendering the spring useless. I have

soldered a thin and flexible silicone isolated laboratory cable from the connection on the relay socket up to the moving arm. Make the connection to the arm close to its tilting line in order to minimize motion in the cable.

### **External Valve Connection Leads**

Two new leads were made from short pieces of suitably isolated cables with moulded on 2.5 mm mono barrel plugs. The outer diameter of this plug is only slightly too thin and was made to fit into the connector panel sockets by soldering a thin strip of copper foil (used for Tiffany glasswork) onto it. The valve connection clip is a battery type (Conrad #736619). See Fig. 3 for details.



Fig. 3 – Barrel plug and valve connection clip



## Tester Panel and Valve Holder Panel

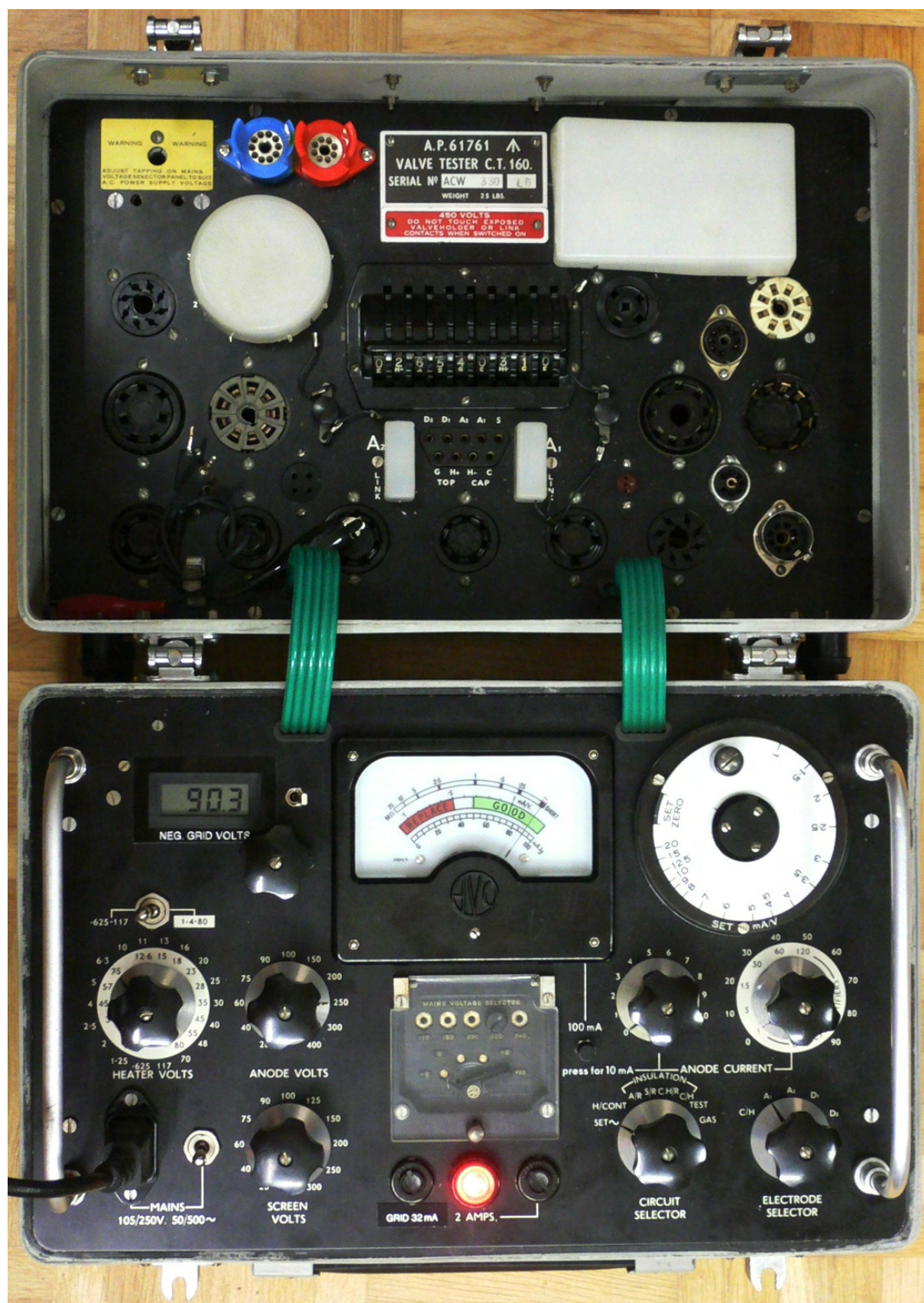


Fig. 4 – Modified tester panel and valve holder panel

The digital meter has been mounted at the position of the original Vg dial. The surrounding anodized aluminium frame covers the hole in the panel behind the scale. The new Vg potentiometer is mounted in place of the bushing for the drive knob of the original dial drive.

The function selector switch is mounted in the existing bore to the right of the former dial. It is toggled horizontally: left pos. = Ug display, right pos. = analogue meter display.

The Anode current range select button is mounted to the right of the voltage selector.

A set of pin straighteners (Dieter Wächter) has been mounted on the valve holder panel in the free space above the covered flying lead valve holder.

A Schuko socket insert has been mounted on the valve holder panel behind the two holes for the mains plug prongs. This will hold the power cord plug when the tester is folded up and stored away.

(Ende)