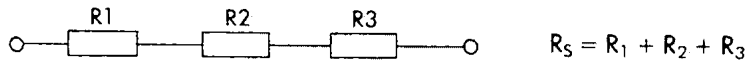



EQUATIONS AND CALCULATIONS

The following (Fig. 6.42) are examples of the electrical/electronic equations and calculations you need to be familiar with.


► Resistors in series




e.g.

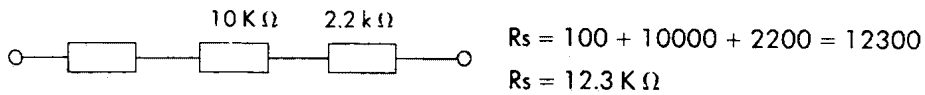

► Resistors in parallel

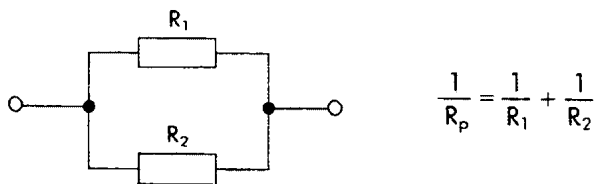

e.g.

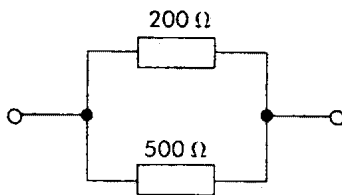


$$\frac{1}{R_p} = \frac{1}{200} + \frac{1}{500}$$

$$\frac{1}{R_p} = \frac{2}{700}$$

$$R_p = \frac{700}{2} \quad R_p = 350 \Omega$$

► Resistors in series and parallel

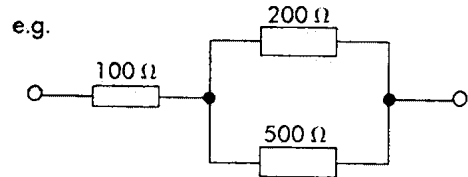

e.g.


$$R_{ps} = 100 + \left(\frac{1}{200} + \frac{1}{500} \right)$$

$$R_{ps} = 100 + \left(\frac{2}{700} \right)$$



$$R_{ps} = 100 + \left(\frac{700}{2} \right)$$

$$R_{ps} = 100 + 350 \quad R_p = 450 \Omega$$

► Capacitors in parallel

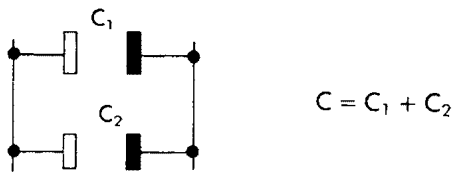

e.g.

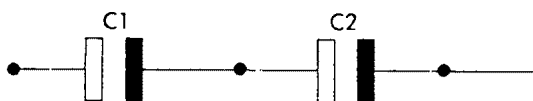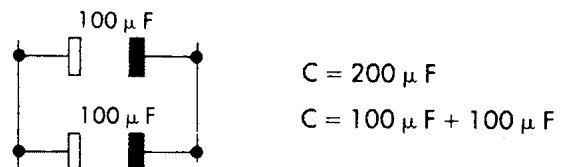

$$\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$\frac{1}{C} = \frac{1}{220} + \frac{1}{220}$$

$$\frac{1}{C} = \frac{1+1}{220} = \frac{2}{220}$$

$$C = \frac{220}{2} = 110 \mu \text{ F}$$

