

PRESENTED FREE
WITH
"PRACTICAL WIRELESS"
NOVEMBER 1961

Practical Wireless 'MINI-AMP' PRICE 5/-

PUBLISHED BY GEO. NEWNES LTD. TOWER HOUSE, SOUTHAMPTON ST., W.C.2.

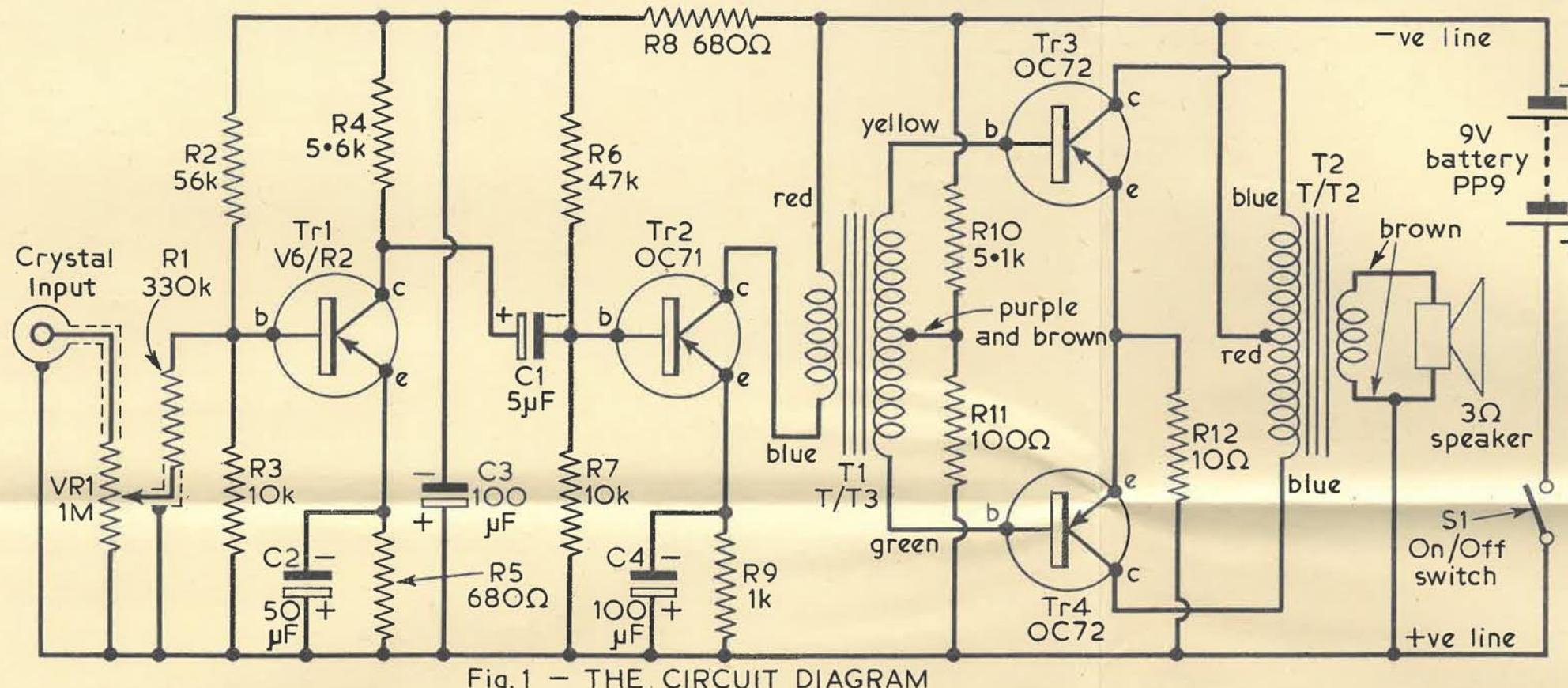


Fig. 1 - THE CIRCUIT DIAGRAM


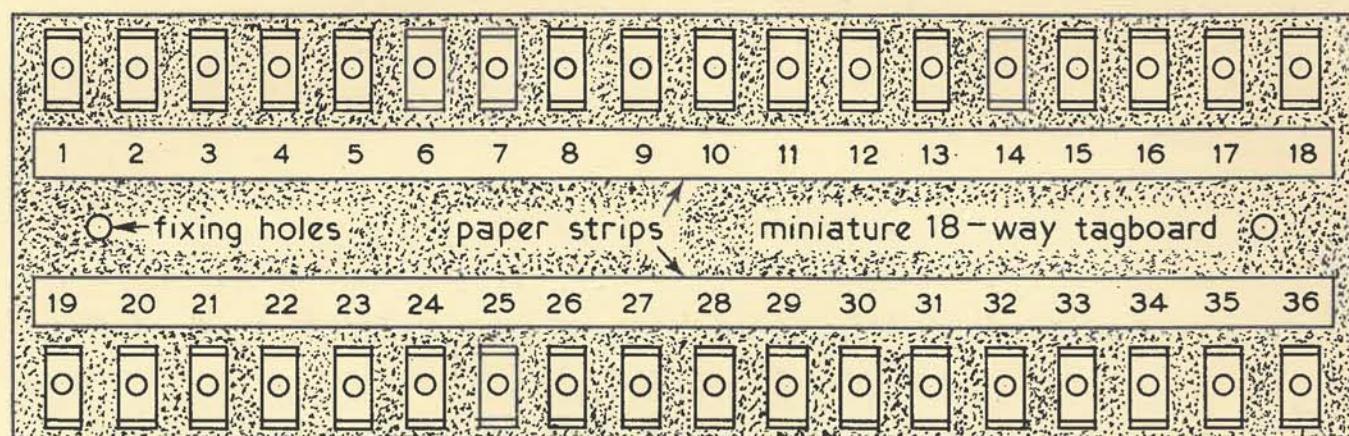


Fig. 2 - NUMBERING THE GROUP-BOARD

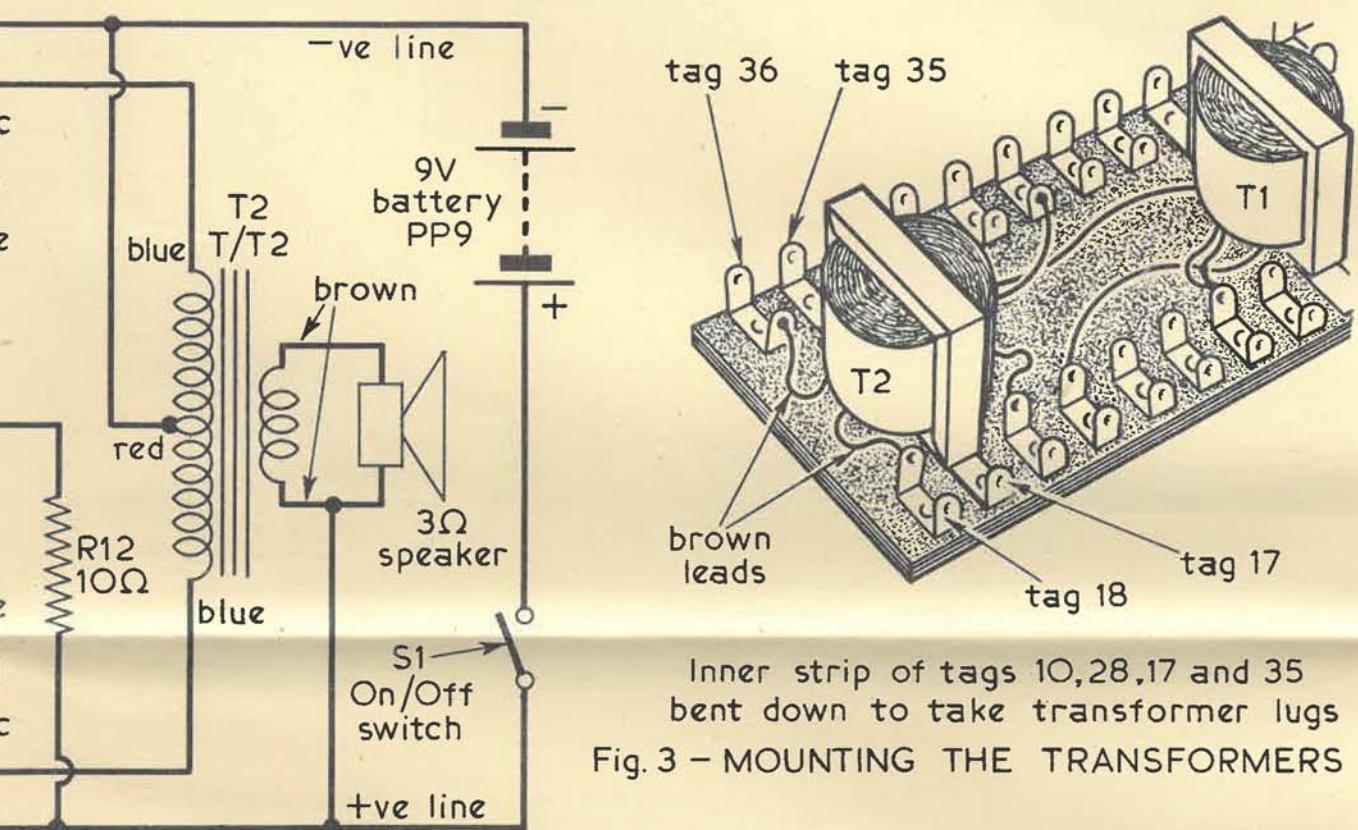

Inner strip of tags 10, 28, 17 and 35 bent down to take transformer lugs

Fig. 3 - MOUNTING THE TRANSFORMERS

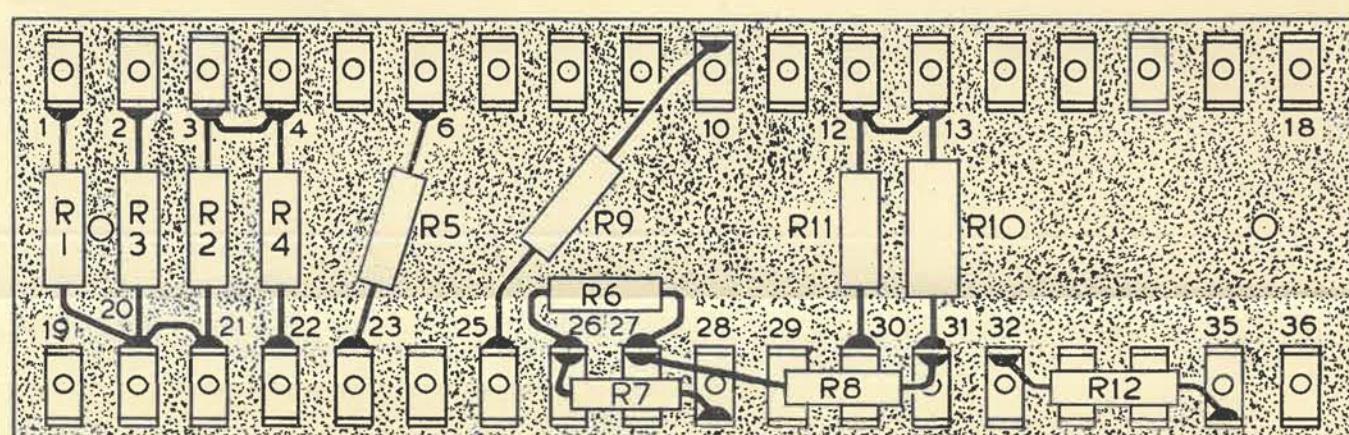


Fig. 5 - WIRING THE RESISTORS

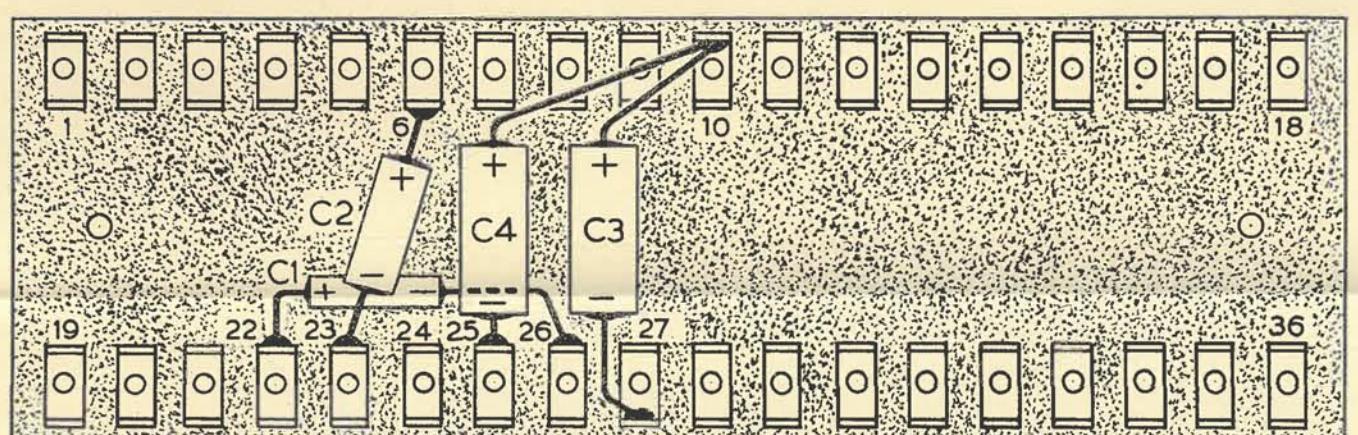


Fig. 6 - WIRING THE CAPACITORS

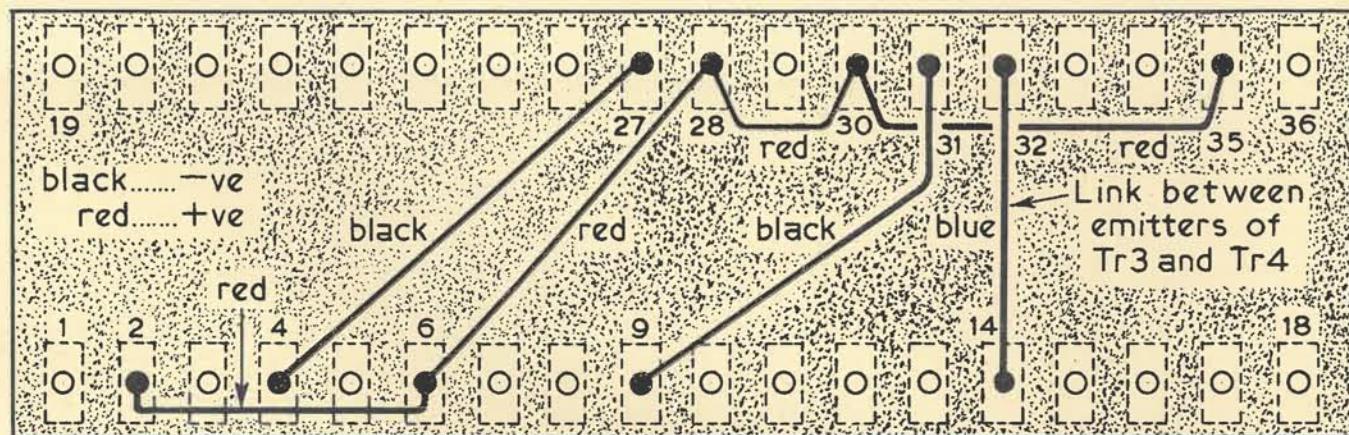


Fig. 7 - WIRING THE CONNECTING LINKS

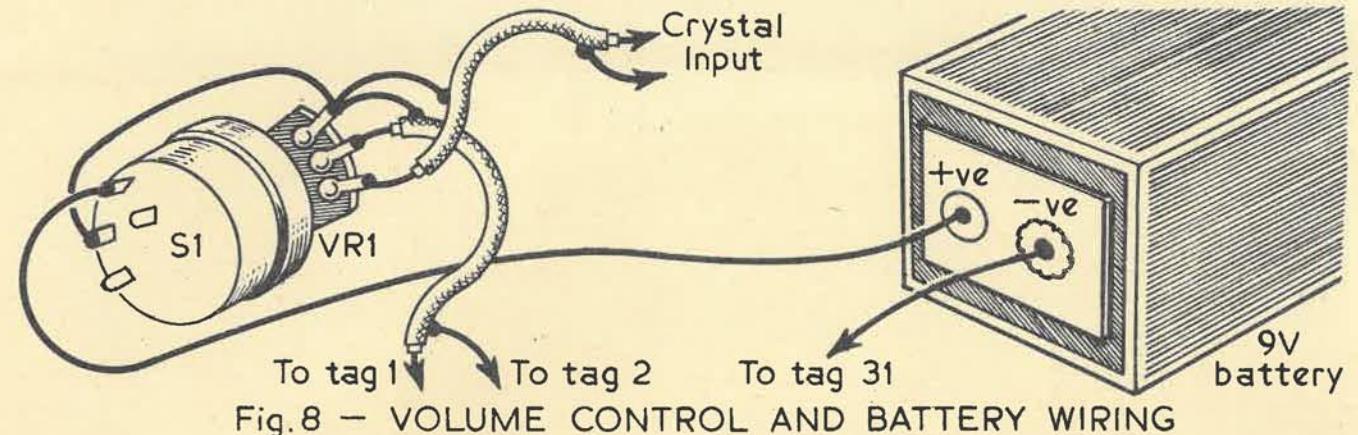


Fig. 8 - VOLUME CONTROL AND BATTERY WIRING

LIST OF PARTS

Resistors
All $\frac{1}{2}$ W and 10% tolerance except R10 and R11
R1.....330k or 220k (1 and 20)
R2.....56k (3 " 21)
R3.....10k (2 " 20)
R4.....5.6k (4 " 22)
R5.....680 Ω (6 " 23)
R6.....47k (26 " 27)
R7.....10k (26 " 28)
R8.....680 Ω (27 " 31)
R9.....1k (10 " 25)
R10.....5.1k 1% or 5% (13 " 31)
R11.....100 Ω 1% or 5% (12 " 30)
R12.....10 Ω (32 " 35)
VR1.....1M Volume control with switch

base
collector
emitter
V6/R2
base
collector
red spot
emitter
OC71, OC72

Capacitors
C1.....5 μ F 15VW (22 and 26)
C2.....50 μ F 15VW (6 " 23)
C3.....100 μ F 15VW (10 " 27)
C4.....100 μ F 15VW (10 " 25)

Transistors
Tr1.....V6/R2 (Newmarket)
Tr2.....OC71 (Mullard)
Tr3, Tr4.....Matched pair of OC72's (Mullard)

Transformers
T1.....Driver Transformer type T/T3 3:6:1+1 (Radiospares)
T2.....Output Transformer type T/T2 3:3+3:3:1 (Radiospares)

Loudspeaker...3in. to 10in., permanent magnet type, 3 Ω to 5 Ω impedance.
Battery....PP9 with two clips to suit (Ever-Ready)

Miscellaneous
18-way tagboard (Radiospares)
Screened cable, connecting wire, solder etc.

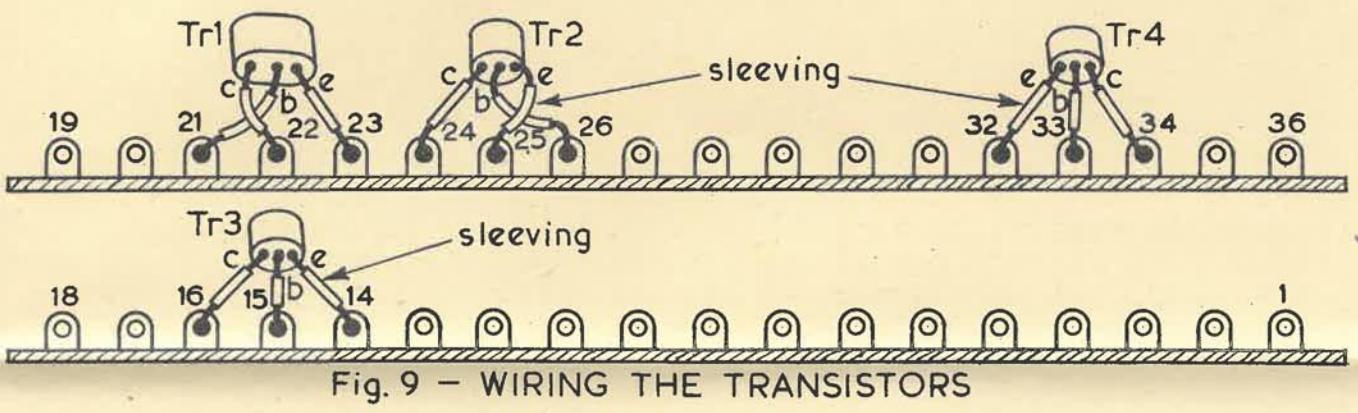


Fig. 9 - WIRING THE TRANSISTORS

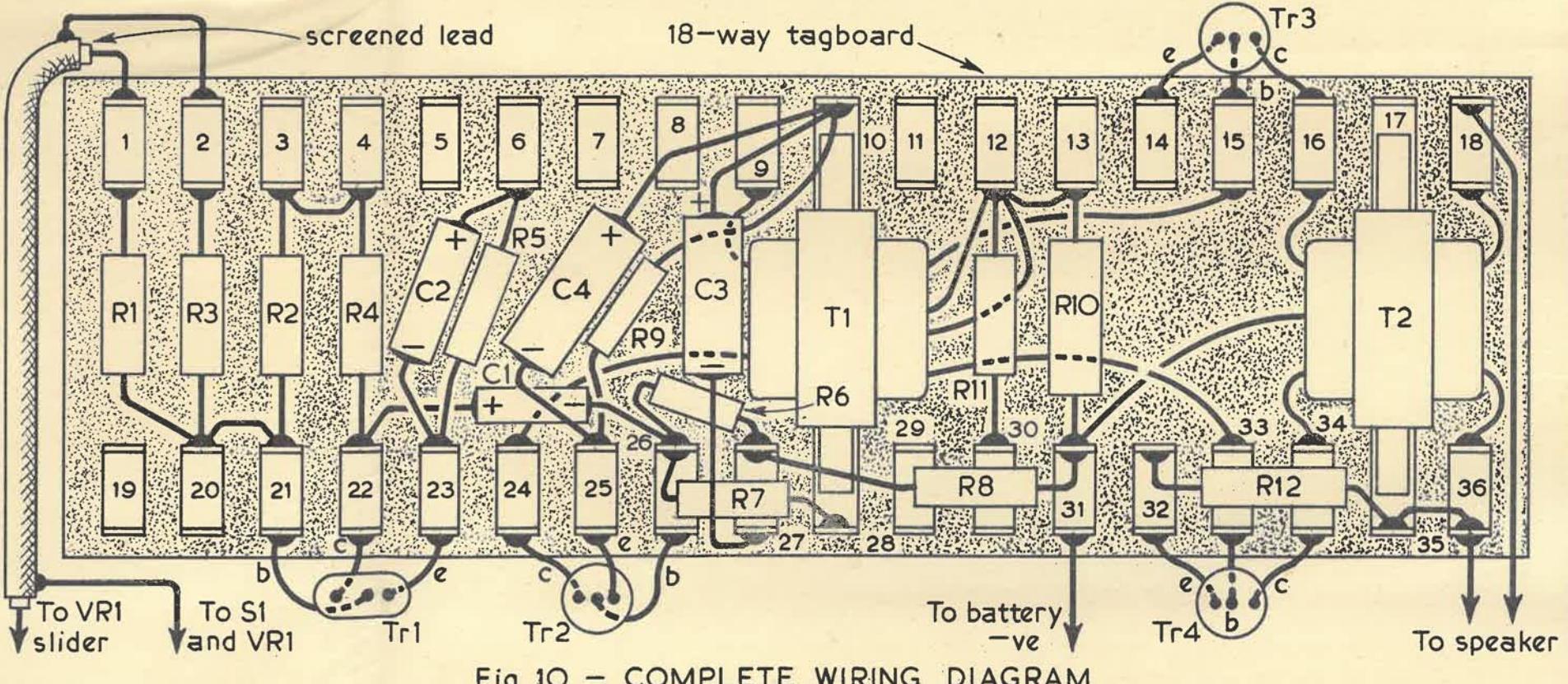


Fig. 10 - COMPLETE WIRING DIAGRAM