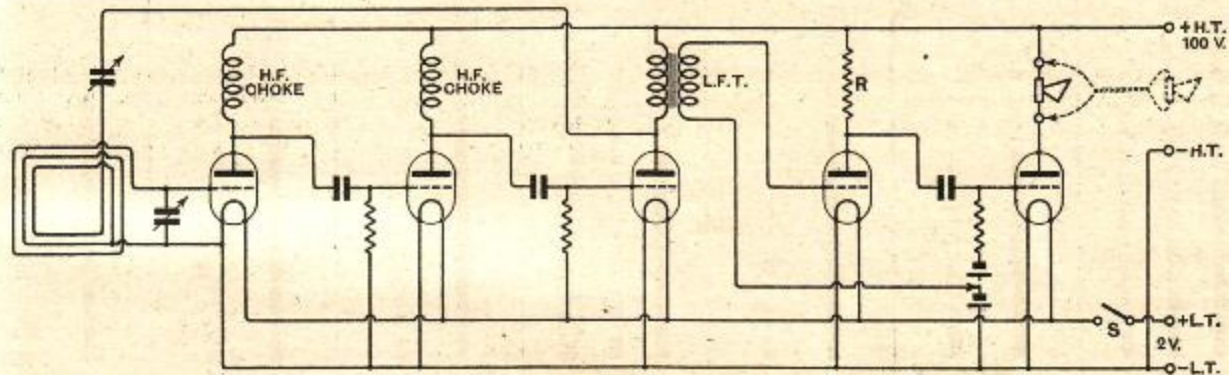
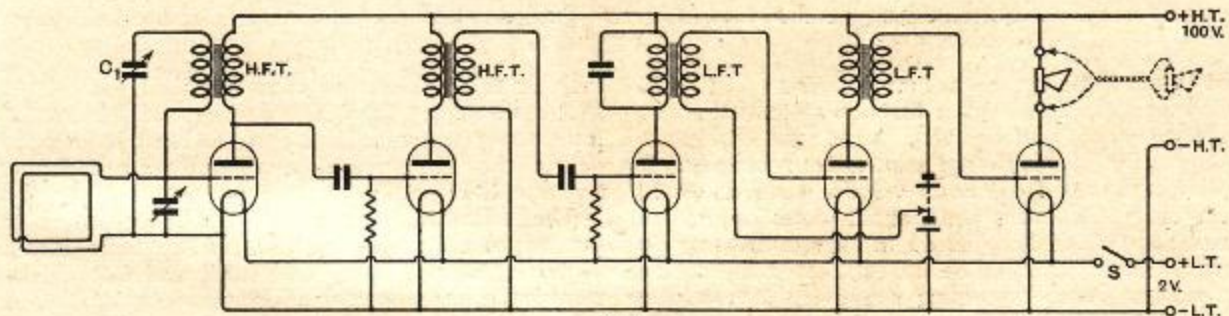




(a)



(b)

Fig. 5.—(a) A popular five-valve circuit used in many portable sets. Aperiodic H.F. chokes are employed. (b) An interesting circuit employing iron-cored high frequency transformers. In dotted lines provision for an external loudspeaker is shown.